

2016

Question 2: Short Questions

- a) Press $M-N$ using r 's complement when $M=2750$ and $N=750$ are in decimal number system.

Answer:

$$\begin{array}{r} M-N \text{ means } 2750 \\ - 750 \\ \hline 2000 \end{array}$$

As base is 10 for decimal number system
so r 's complement will be 10's complement

$$\begin{array}{r} 2750 \text{ --- } (1) \\ 750 \text{ --- } (1) \end{array}$$

Take 10's complement of (1)

$$\begin{array}{r} 9999 \\ - 750 \\ \hline 9249 \\ + 1 \\ \hline 9250 \text{ --- } (11) \end{array}$$


Add (1) and (11) ①

$$\begin{array}{r} 2750 \\ + 9250 \\ \hline 12000 \end{array}$$

Carry drop $\leftarrow 1/2000$ Ans

 b) Design 4:1 Multiplexer.

Answer To construct a 4:1 MUX, we need 2 selection lines let suppose S_0 and S_1 .



It will select one input from the input lines according to selection lines data.

c) Express the given functions in a sum of minterms and a product of maxterms.

Answer

$$F(A, B, C, D) = D(A' + B) + B'D$$

$$F(A, B, C, D) = A'D + BD + B'D \quad \text{For SOP}$$

POS is a complement of SOP, so

$$F(A, B, C, D) = \overline{(A'D) + (BD) + (B'D)}$$

$$\begin{aligned} &= (\overline{A'D}) \cdot (\overline{BD}) \cdot (\overline{B'D}) \\ &= (\overline{A} + \overline{D}) \cdot (\overline{B} + \overline{D}) \cdot (\overline{B} + \overline{D}) \\ &= (A + D) \cdot (\overline{B} + \overline{D}) \cdot (B + \overline{D}) \quad \text{Ans} \end{aligned}$$

d) Draw the truth table of Half Adder circuit?
Answer


| Inputs | | Outputs | |
|--------|---|---------|-------|
| A | B | Sum | Carry |
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

e) Draw a circuit for given function using NAND gate only.

$$F(X, Y, Z) = XY + X'Z$$


Answer:

First draw the circuit,

 


Add (0) inverter on inputs of OR gate and output of AND gates and replace NOT gate with (~~Do~~) to (~~Do~~)

So,

 

Replace ~~AND~~ with ~~OR~~

 

required circuit
with NAND gates only

f) What is the difference between ROM and RAM?

Answers

RAM

- Stands for Random Access Memory
- It is a volatile memory.
- Can do both read and write operations
- memory capacity is upto 256 gb per chip.
- The data stored in RAM is lost in case of power failure.

ROM

- stands for Read Only Memory.
- It is a ^{non}-volatile memory.
- Can do only read operations.
- memory capacity is upto 4 to 8 MB per chip
- The data in ROM doesn't lose in case of power failure

g) Give the excitation table for JK flipflop.
 Answer

Excitation Table is:


| Present State | Next State | Inputs | |
|---------------|------------|--------|---|
| Q_n | Q_{n+1} | J | K |
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | X |
| 1 | 0 | X | 1 |
| 1 | 1 | X | 0 |

Question 3: Long Questions

 a) Design a counter with the following binary sequences: 0, 1, 3, 7, 6, 4 and repeat. Use JK-FlipFlops.

Answer

3-bit Synchronous counter will be used for this sequence with the help of JK FlipFlops. 3-bits means 3 FlipFlops will be used.



Transition Tables

| Present State | | | Next State | | | Inputs | | | |
|---------------|-------|-------|------------|--------|--------|------------|------------|------------|--|
| Q_2 | Q_1 | Q_0 | Q_2' | Q_1' | Q_0' | J_2, K_2 | J_1, K_1 | J_0, K_0 | |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 X | 0 X | 1 X | |
| 0 | 0 | 1 | 0 | 1 | 1 | 0 X | 1 X | X 0 | |
| 0 | 1 | 1 | 1 | 1 | 1 | 1 X | X 0 | X 0 | |
| 1 | 1 | 1 | 1 | 1 | 0 | X 0 | X 0 | X 1 | |
| 1 | 1 | 0 | 1 | 0 | 0 | X 0 | X 1 | 0 X | |
| 1 | 0 | 0 | 0 | 0 | 0 | X 1 | 0 X | 0 X | |

Now, we have to find the values of J_2, J_1, J_0 and K_2, K_1, K_0 in terms of Q_2, Q_1, Q_0 using K-maps

J_2

| $Q_2 \backslash Q_0$ | 00 | 01 | 11 | 10 |
|----------------------|----|----|----|----|
| 0 | 0 | 0 | 1 | 0 |
| 1 | X | 0 | X | X |

$$J_2 = Q_1 Q_0$$

K_2

| $Q_2 \backslash Q_0$ | 00 | 01 | 11 | 10 |
|----------------------|----|----|----|----|
| 0 | X | X | X | 0 |
| 1 | 1 | 0 | 0 | 0 |

$$K_2 = Q_1' Q_0'$$

~~J_1~~

| $Q_2 \backslash Q_0$ | 00 | 01 | 11 | 10 |
|--------------------------------------------|---------------|---------------|---------------|---------------|
| 0 | 0 | 1 | X | |
| 1 | 0 | | X | X |

~~$$J_1 = Q_1 Q_0$$~~

K_1

| $Q_2 \backslash Q_0$ | 00 | 01 | 11 | 10 |
|----------------------|----|----|----|----|
| 0 | X | X | | |
| 1 | X | | | 1 |

$$K_1 = Q_2 Q_0'$$

J_1
 $Q_2 \quad Q_1 Q_0$

| | | | | |
|---|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 0 | | 1 | X | |
| 1 | | | X | X |

$$J_1 = Q_2' Q_0$$

J_0
 $Q_2 \quad Q_1 Q_0$

| | | | | |
|---|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 0 | 1 | X | X | |
| 1 | | | X | |


$$J_0 = Q_2' Q_1'$$

K_0
 $Q_2 \quad Q_1 Q_0$

| | | | | |
|---|----|----|----|----|
| | 00 | 01 | 11 | 10 |
| 0 | X | | | |
| 1 | X | | 1 | X |

$$K_0 = Q_2 Q_1$$

Circuit Diagrams

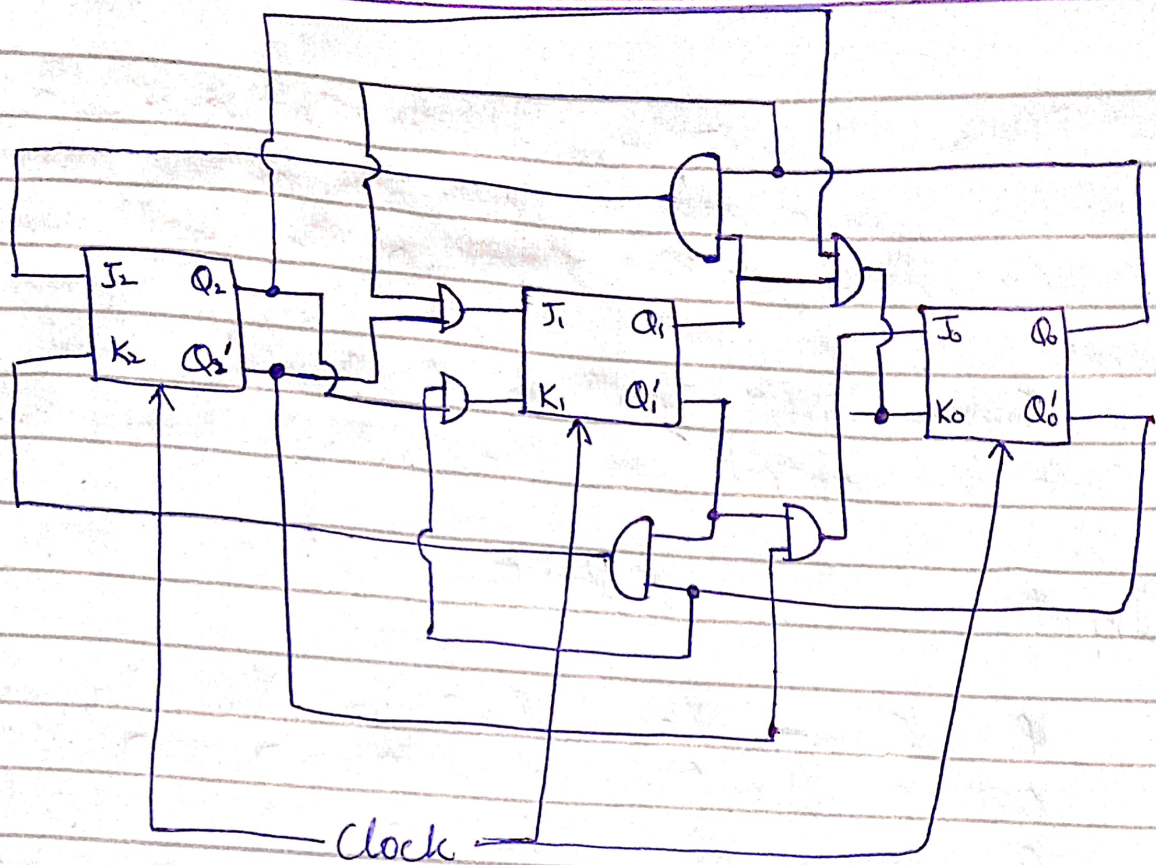

b) Design a combinational circuit that accepts a 3-bit number and generates an output binary number equal to the square of the input number.

Answers

Suppose 3-bit input as A, B and C and 6-bit output as X_5, X_4, X_3, X_2, X_1 and X_0 .

Inputs

Outputs

| A | B | C | X_5 | X_4 | X_3 | X_2 | X_1 | X_0 |
|---|---|---|-------|-------|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 |

$$X_5 = ABC' + ABC = AB(C + C') = AB$$

$$\begin{aligned} X_4 &= ABC + AB'C + AB'C' = ABC + AB'(C + C') \\ &= ABC + AB' = A(BC + B') = A(B + B')(B' + C) \\ &= A(B' + C) = AB' + AC \end{aligned}$$


$$X_3 = A'BC + AB'C = C(A'B + AB') = C(A \oplus B)$$

$$X_2 = A'BC' + ABC' = BC'(A' + A) = BC'$$

$$X_1 = 0$$

$$\begin{aligned} X_0 &= A'B'C + A'BC + AB'C + ABC \\ &= A'C(B'+B) + AC(B'+B) \\ &= A'C + AC = C(A'+A) \\ X_0 &= C \end{aligned}$$

Circuit Diagrams

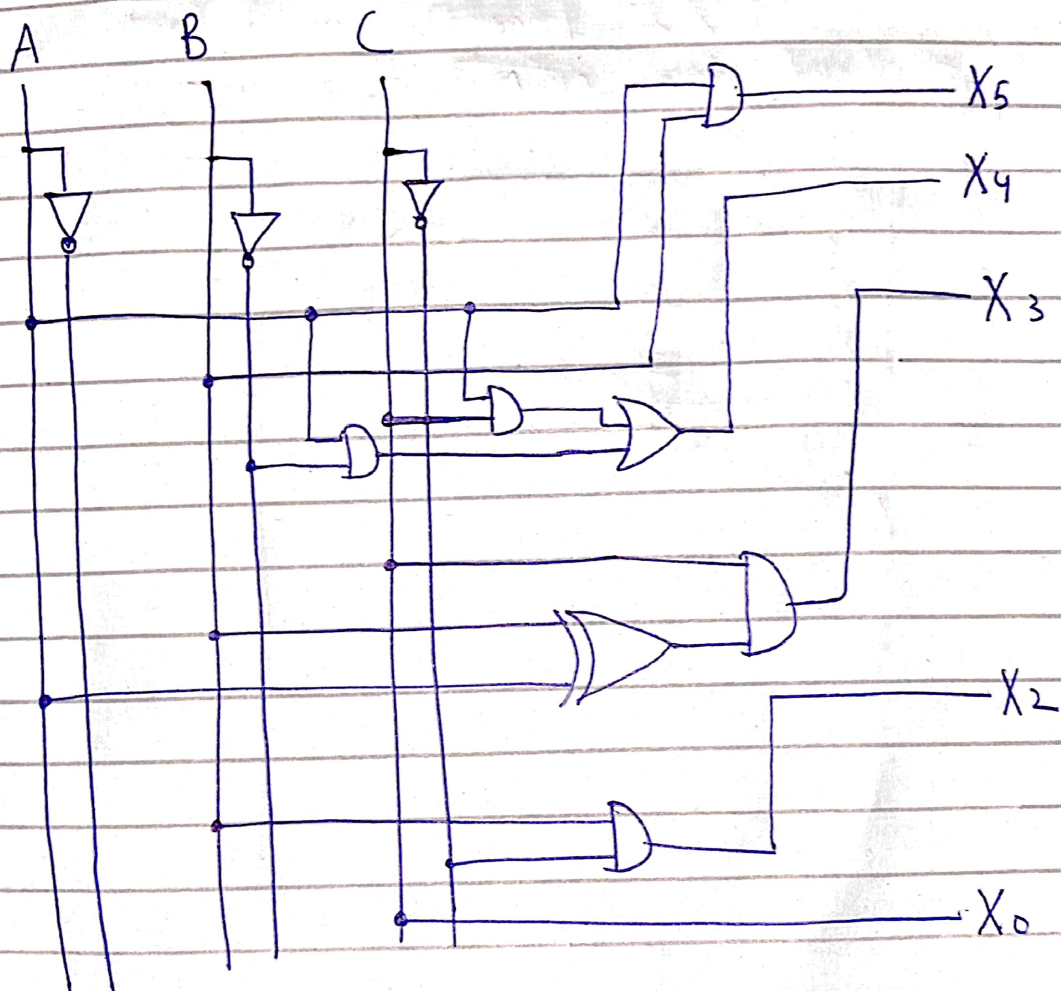

Date: _____

Day: MTWTFS

Full Subtractor

3 inputs 2 outputs 8 difference
borrow


3 inputs = $2^3 = 8$ combinations

| X | Y | Z | D | B |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

$$\begin{aligned} D &= \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ \\ &= \bar{X}(\bar{Y}Z + Y\bar{Z}) + X(\bar{Y}\bar{Z} + YZ) \\ &= \bar{X}(Y \oplus Z) + X(Y \odot Z) \\ &= \bar{X}(Y \oplus Z) + X(\overline{Y \oplus Z}) \\ &= X \oplus (Y \oplus Z) \end{aligned}$$

$$\begin{aligned} B &= X'Y'Z + X'YZ' + X'YZ + XYZ \\ &= X'(Y'Z + YZ') + YZ(X + X') \\ &= X'(Y \oplus Z) + YZ \end{aligned}$$

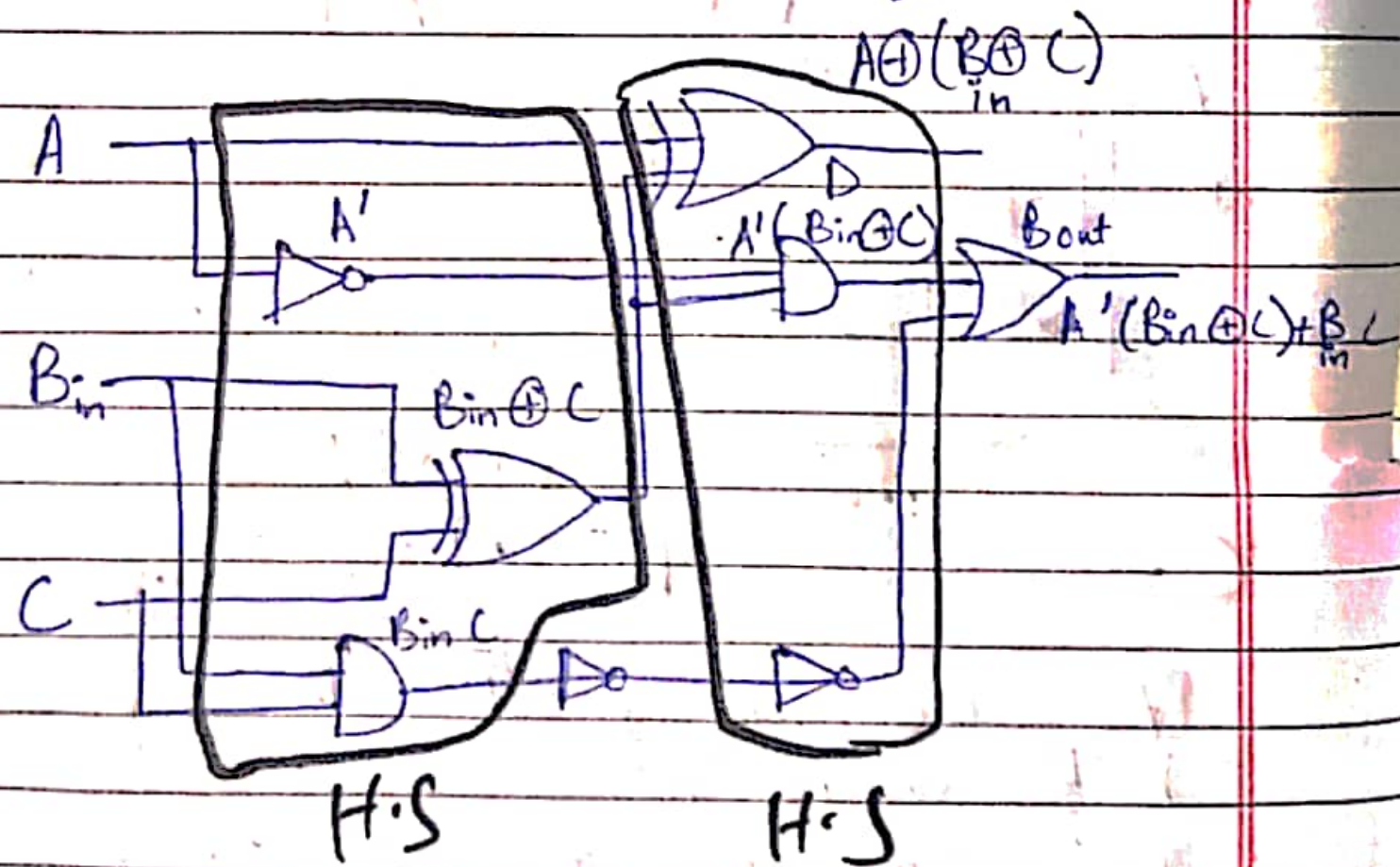Full Subtractor with Two Half Subtractors:



c) ii) Draw 4×2 Encoder circuit.

Answer:

Encoder is a combinational circuit having 2^n input lines and n output lines

$$2^n \times n$$

So, 4×2 Encoder will have four inputs and two outputs.

